

Q1.

- When we divided the time duration  $T$  into discrete time intervals of length  $h$  each, we then have  $n+1$  time instances, with  $x_i, v_i, a_i, k_i, p_i$  for each of them. We know that  $x_i, a_i, k_i, p_i, p_{d,i}$  are all related to  $v_i$ , hence we can set  $v_i$  (velocity) and  $p_{b,i}$  (braking power) as our decision variables.

The optimisation problem, then becomes the following:

$$\min h \sum_{r=0}^{n-1} p_r$$

$$\text{s.t. } x_0 = 0$$

$$x_n \geq x_f$$

$$a_r \leq A \quad \forall r = \{0, 1, 2, \dots, n-1\}$$

$$0 \leq v_r \leq V \quad \forall r = \{0, 1, 2, \dots, n-1\}$$

$$v_n \leq v_f$$

subject to

$$x_{r+1} = x_r + h \frac{(v_r + v_{r+1})}{2} \quad \forall r = \{0, 1, \dots, n-1\}$$

$$a_r = \frac{v_{r+1} - v_r}{h} \quad \forall r = \{0, 1, \dots, n-1\}$$

$$p_{d,r} = c v_r^3 \quad \forall r = \{0, 1, 2, \dots, n-1\}$$

$$p_r = p_{b,r} + p_{d,r} + \frac{(k_{r+1} - k_r)}{h} \quad \forall r = \{0, 1, \dots, n-1\}$$

$$k_r = \frac{v_r^2}{2} \quad \forall r = \{0, 1, 2, \dots, n\}$$

2. Done in Code

3. The constraints with equality are not convex, i.e.

$p_{d,r} = c v_r^3$  and  $k_r = v_r^2/2$ . If we rephrase them as:  $p_{d,r} \geq c v_r^3$  and  $k_r \geq v_r^2/2$ , which are convex on  $v_r \geq 0$ .  
 $\Rightarrow$  At optimal case, inequalities will be tight.

Q2.

Since we know that  $f_k$  is non-decreasing, we have

$$\int_0^{i_k} f(u_k) du_k \text{ is convex in } i_k.$$

Our optimisation problem is:

$$\text{minimize } \phi(i)$$

$$\text{s.t. } Ai = 0$$

$$\text{with } i \in \mathbb{R}^m$$

Consider a dual variable associated as  $p$ :

$$Ai = 0 \quad \text{and} \quad \nabla \phi(i) + A^T p = 0$$


$$\text{Let } v = \nabla \phi(i) \text{ and } e = -p$$

$\Rightarrow$  Optimality conditions (dual):

$$Ai = 0 \quad A^T e = v \quad v_k = f_k(i_k) \quad k=1, 2, \dots, m$$



### 3. Circuit 'a':

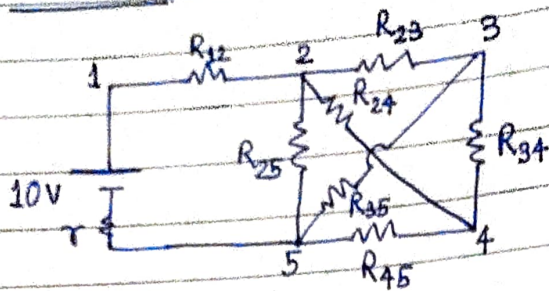

Given that,  $R_{12} = R_{34} = R_{35} = R_{24} = R_{25} = 10 \Omega$

and  $R_{23} = R_{45} = 100 \Omega$

and  $r = 2 \Omega$ ,  $V = 10V$

$\Rightarrow i \in \mathbb{R}^8$  and  $A \in \mathbb{R}^{5 \times 8}$

We obtain:

$$A = \begin{bmatrix} +1 & 0 & 0 & 0 & 0 & 0 & 0 & -1 \\ -1 & 1 & 0 & 0 & 1 & 0 & 1 & 0 \\ 0 & -1 & 1 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & -1 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & 0 & -1 & -1 & 1 \end{bmatrix}$$

Some results (useful in circuit 'b' too):

- For  $v_k = i_k R_k$  (resistor)  $\Rightarrow \int_0^{i_k} z_k R_k dz_k = \frac{i_k^2 R_k}{2}$
- For  $v_k = V_k + i_k r_k \Rightarrow \int_0^{i_k} (V_k + z_k r_k) dz_k = V_k i_k + \frac{i_k^2 r_k}{2}$
- For  $v_k = V_T \log\left(1 + \frac{i_k}{I_s}\right) \Rightarrow \int_0^{i_k} V_T \log\left(1 + \frac{z_k}{I_s}\right) dz_k =$   
 $= V_T I_s \left( \left(1 + \frac{i_k}{I_s}\right) \log\left(1 + \frac{i_k}{I_s}\right) - \frac{i_k}{I_s} \right)$

For circuit 'a':

$$\phi(i) = -V_B i_8 + \frac{i_8^2 r}{2} + \frac{i_1^2 R_1}{2} + \frac{i_2^2 R_2}{2} + \frac{i_3^2 R_3}{2} \\ + \frac{i_4^2 R_4}{2} + \frac{i_5^2 R_5}{2} + \frac{i_6^2 R_6}{2} + \frac{i_7^2 R_7}{2}$$

The primal and dual for the circuit 'a' are:

Primal:  $\min \phi(i)$   
s.t.  $Ai = 0$


Dual:  $\max_b L(i, b)$

s.t.  $Ai = 0 \quad A^T e = v \quad (b = -e)$

$\Rightarrow A^T b = -v$

and  $V_k = \begin{cases} i_k R_k & \text{for } k=1, 2, \dots, 7 \\ V_k + i_k r_k & \text{for } k=8 \end{cases}$

Circuit 'b':

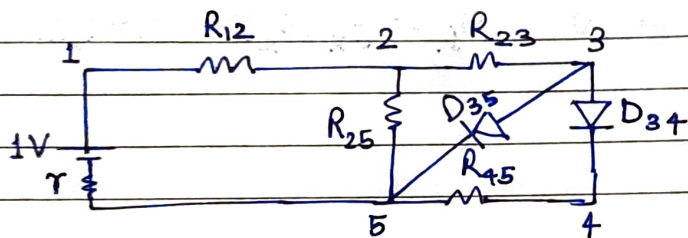

Given:  $R_{12} = R_{23} = R_{25} = 1000 \Omega$

and  $R_{45} = 100 \Omega$

and for diodes  $D_{34}, D_{35}$ :  $V_T = 30 \times 10^{-3} V$

$I_s = 0.5 mA$

$\Rightarrow i \in \mathbb{R}^7$  and  $A \in \mathbb{R}^{5 \times 7}$

We obtain:

$$A = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & -1 \\ -1 & 1 & 0 & 0 & 0 & 1 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & -1 & -1 & 1 \end{bmatrix}$$



for circuit 'b':

$$\begin{aligned}\phi(i) = & -V_7 i_7 + \frac{i_7^2 R}{2} + V_T I_s \left( \left(1 + \frac{i_3}{I_s}\right) \log\left(1 + \frac{i_3}{I_s}\right) - \frac{i_3}{I_s} \right) \\ & + V_T I_s \left( \left(1 + \frac{i_5}{I_s}\right) \log\left(1 + \frac{i_5}{I_s}\right) - \frac{i_5}{I_s} \right) \\ & + \sum_k \frac{i_k^2 R_k}{2} \\ & \quad \downarrow \\ & \quad k = 1, 2, 4, 6\end{aligned}$$

The primal and dual for circuit 'b' are:

Primal:  $\min \phi(i)$   
s.t.  $Ai = 0$

Dual:  $\max_b L(i, b)$   
s.t.  $Ai = 0 \quad -v = A^T b$

$$V_k = \begin{cases} i_k R_k & \text{for } k = 1, 2, 4, 6 \leftarrow \text{Resistor} \\ V_k + i_k R_k & \text{for } k = 7 \leftarrow \text{Battery} \\ V_T \log\left(1 + \frac{i_k}{I_s}\right) & \text{for } k = 3, 5 \leftarrow \text{Diode} \end{cases}$$